

Low-Cost I²C Level Translator

1. Introduction

This applications note discusses a low-cost circuit for I²C level translation. This circuit was developed for the Si701x, Si702x, and Si703x humidity sensors but will work in many applications.

This circuit provides I²C level translation from a higher voltage supply, such as 5 V, to a lower voltage, supply such as 1.8 or 3.3 V. In addition, the optional emitter follower circuit provides a low-voltage power supply rail from the higher 5 V supply.

Note that some devices allow for higher voltage tolerance on I²C inputs. For example, the Si7034 has a 3.3 V tolerant I²C interface, so the level translation is only required for 5 V I²C designs.

2. Circuit

The basic circuit is shown in Figure 1.

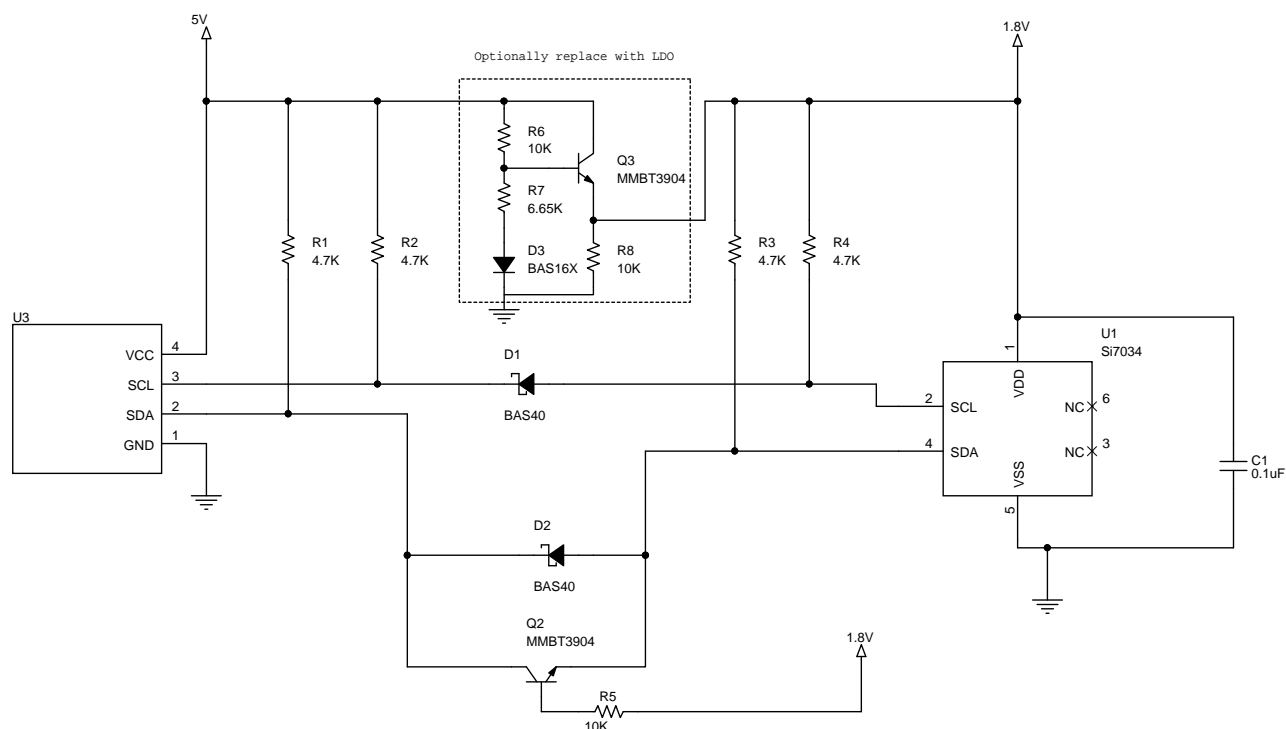


Figure 1. Low-Cost I²C Level Translator Circuit

In this case, we are translating from 5 V to 1.8 V, and the I²C speed is assumed to be sufficiently slow for clock stretching to not occur (i.e. less than 300 kHz for the Si701x, Si702x, and Si703x humidity sensors). In this case, the SCL line is unidirectional.

For the SCL line, a Schottky diode is used to prevent the SCL line from pulling all the way high on the lower voltage device while allowing it to pull all the way high on the higher voltage device. The voltage drop across the Schottky diode must be low enough so that when the higher-voltage device pulls low, there is still a logic low on the lower-voltage device. For the Si7034 used in this case, the logic low level is 0.54 V ($0.3 \times V_{DD}$), and the Schottky diode drop is about 0.35 V, so there is no issue. If the lower voltage device was on a 3.3 V rail, an ordinary diode could be used.

The SDA line is bidirectional, and Q2 is added so that when the lower voltage device pulls down on SDA, SDA of the higher voltage device will pull down. In a case where clock stretching needs to be supported, SCL can be made bidirectional by adding the same transistor circuit across D1.

The emitter follower circuit is a low-cost method for providing a 1.8 V rail from the higher 5 V supply. Alternatively, this circuit can be replaced with an LDO for a simpler layout or if additional voltage regulation is required.

3. Waveforms

The circuit was tested for the case of 3.3 to 1.8 V level translation. Figure 2 shows the waveforms on the SDA line with a clean translation from 3.3 V (blue trace) to 1.8 V (yellow trace).



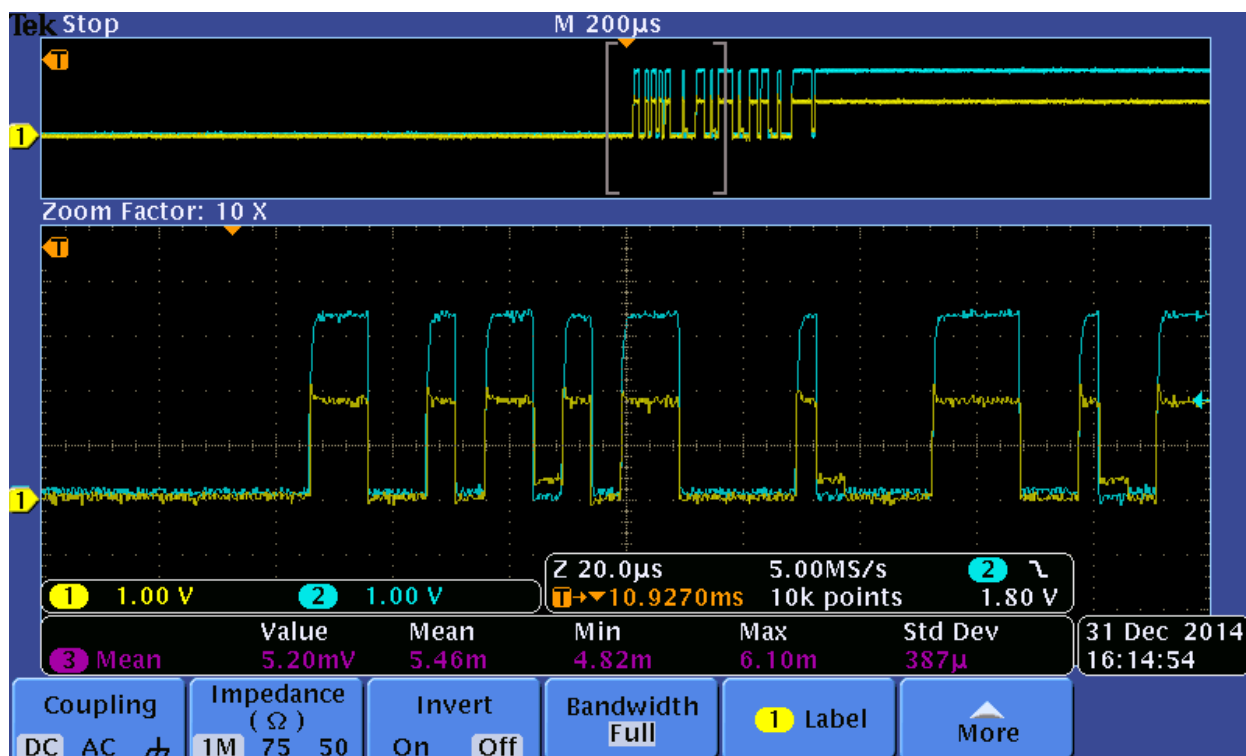


Figure 2. SDA Line at 1 V per Division

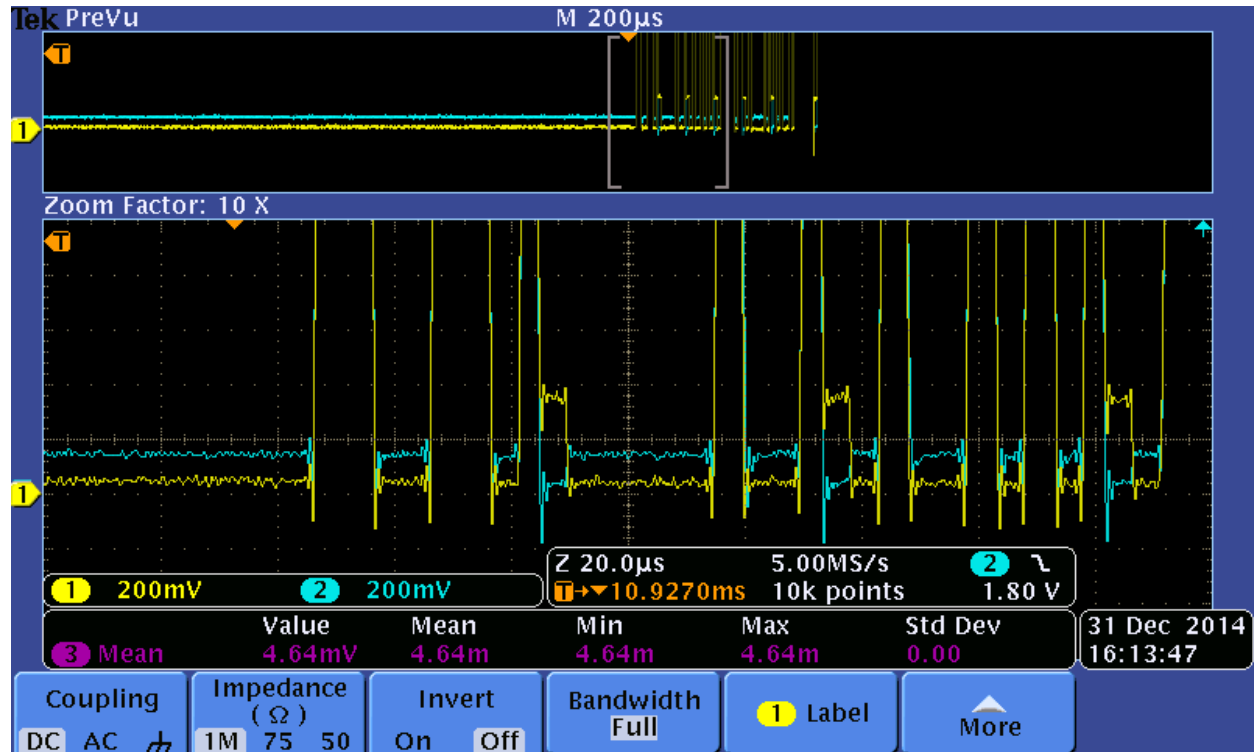Zooming in to 200 mV per division, the circuit operation can be clearly seen in Figure 3.



4. Conclusion

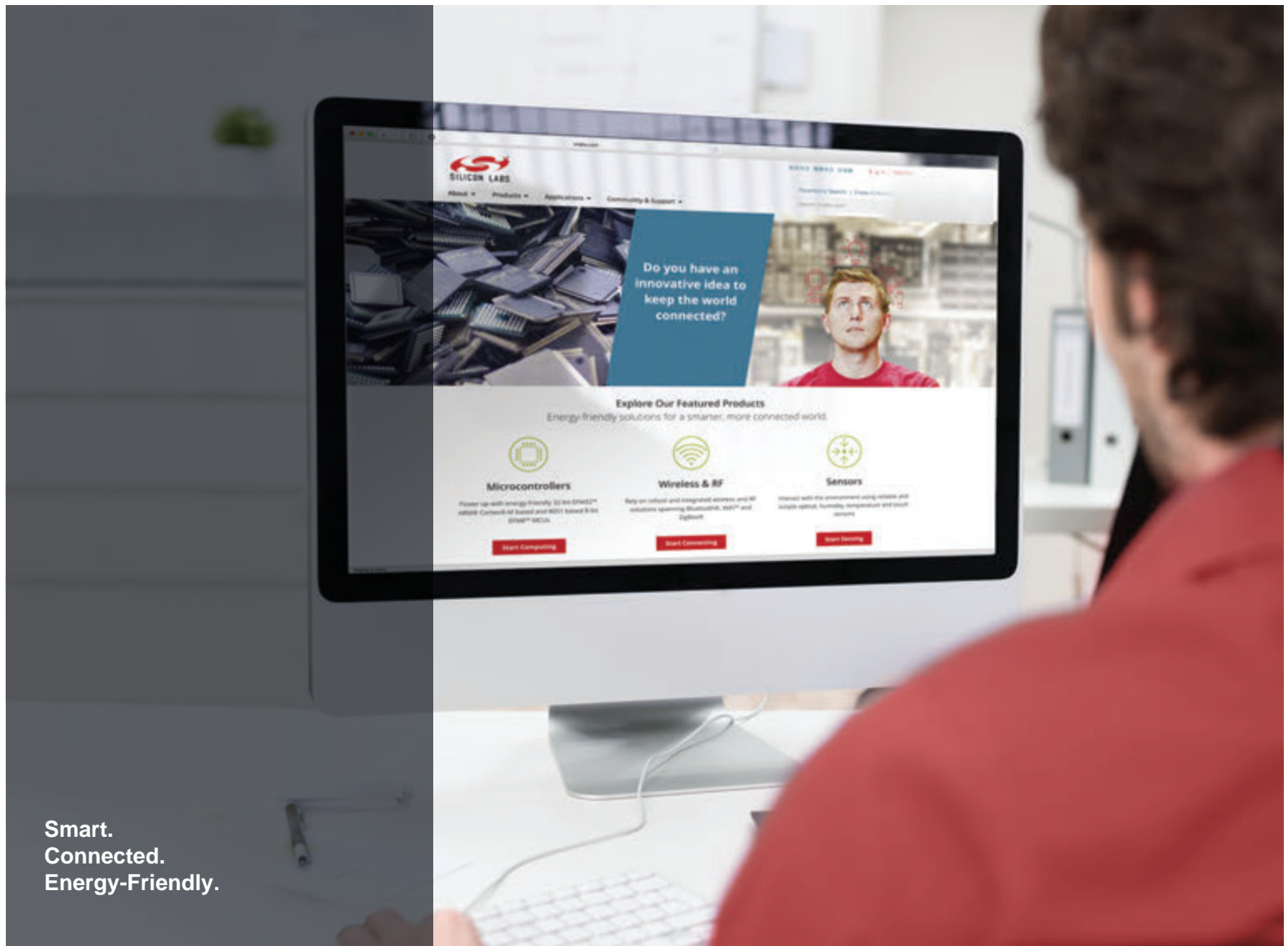

Smart.
Connected.
Energy-Friendly.



Products
www.silabs.com/products



Quality
www.silabs.com/quality



Support and Community
community.silabs.com

Disclaimer

Silicon Laboratories intends to provide customers with the latest, accurate, and in-depth documentation of all peripherals and modules available for system and software implementers using or intending to use the Silicon Laboratories products. Characterization data, available modules and peripherals, memory sizes and memory addresses refer to each specific device, and "Typical" parameters provided can and do vary in different applications. Application examples described herein are for illustrative purposes only. Silicon Laboratories reserves the right to make changes without further notice and limitation to product information, specifications, and descriptions herein, and does not give warranties as to the accuracy or completeness of the included information. Silicon Laboratories shall have no liability for the consequences of use of the information supplied herein. This document does not imply or express copyright licenses granted hereunder to design or fabricate any integrated circuits. The products are not designed or authorized to be used within any Life Support System without the specific written consent of Silicon Laboratories. A "Life Support System" is any product or system intended to support or sustain life and/or health, which, if it fails, can be reasonably expected to result in significant personal injury or death. Silicon Laboratories products are not designed or authorized for military applications. Silicon Laboratories products shall under no circumstances be used in weapons of mass destruction including (but not limited to) nuclear, biological or chemical weapons, or missiles capable of delivering such weapons.

Trademark Information

Silicon Laboratories Inc.®, Silicon Laboratories®, Silicon Labs®, SiLabs® and the Silicon Labs logo®, Bluegiga®, Bluegiga Logo®, Clockbuilder®, CMEEMS®, DSPLL®, EFM®, EFM32®, EFR®, Ember®, Energy Micro, Energy Micro logo and combinations thereof, "the world's most energy friendly microcontrollers", Ember®, EZLink®, EZRadio®, EZRadioPRO®, Gecko®, ISOModem®, Precision32®, ProSLIC®, Simplicity Studio®, SiPHY®, Telegesis, the Telegesis Logo®, USBXpress® and others are trademarks or registered trademarks of Silicon Laboratories Inc. ARM, CORTEX, Cortex-M3 and THUMB are trademarks or registered trademarks of ARM Holdings. Keil is a registered trademark of ARM Limited. All other products or brand names mentioned herein are trademarks of their respective holders.



Silicon Laboratories Inc.
400 West Cesar Chavez
Austin, TX 78701
USA

<http://www.silabs.com>